 


無線通訊系統 之積體電路設計(I)

Ron-Yi Liu

Tel: (O) 03-4245950,
最好使用 Email: ryliu@cht.com.tw



Outline

- Introduction of Wireless Communication System
- Analog Filter Design
- Switched Capacitor Filter Design
- Digital to Analog Circuit Design
- S/H Circuit Design
- Analog to Digital Circuit Design
- Appendix

Systems: from 1946 to 2005

1-5

2010/5/3

Ron-Yi Liu



Original ENIAC machine at University of Pennsylvania
Speed: 5,000 additions or 10 multiplications/sec
* 17,500 vacuum tubes
* 174 KW
* 18,000 sq ft



INTEL P4, 90 nm CMOS
In this technology, it has:
-Area: 30x30 μm
-Power @ 1 MHz: 1 μW
-Potential speed: ~10 GHz


Wireless Integrated Microsystems (WIMS)

1-6


2010/5/3

Ron-Yi Liu

Environmental Sensors

 

Heavy Metals

 


μ Gas Chromatograph

Biomedical Implants



Cochlear Implant

 

Deep Brain Implants

2002 and Beyond

1-7

2010/5/3

Ron-Yi Liu

Semiconductor Industry Association (SIA) Road Map, 1998 Update

	1999	2002	2014
Technology (nm)	180	130	35
Minimum mask count	22/24	24	29/30
Wafer diameter (mm)	300	300	450
Memory-samples (bits)	1G	4G	1T
Transistors/cm ² (μ P)	6.2M	18M	390M
Wiring levels (maximum)	6-7	7	10
Clock, local (MHz)	1,250	2,100	10,000
Chip size: DRAM (mm ²)	400	560	2240
Chip size: mP (mm ²)	340	430	901
Power supply (V)	1.5-1.8	1.2-1.5	0.37-0.42
Maximum Power (W)	90	130	183
Number of pins (μ P)	700	957	3,350

IEEE Spectrum, July 2009

Special report: "The 100-million transistor IC"


These scaling trends will allow the electronics market to growth at 15% / year.

The Evolution of Cellular Phone

1-8

2010/5/3

Ron-Yi Liu

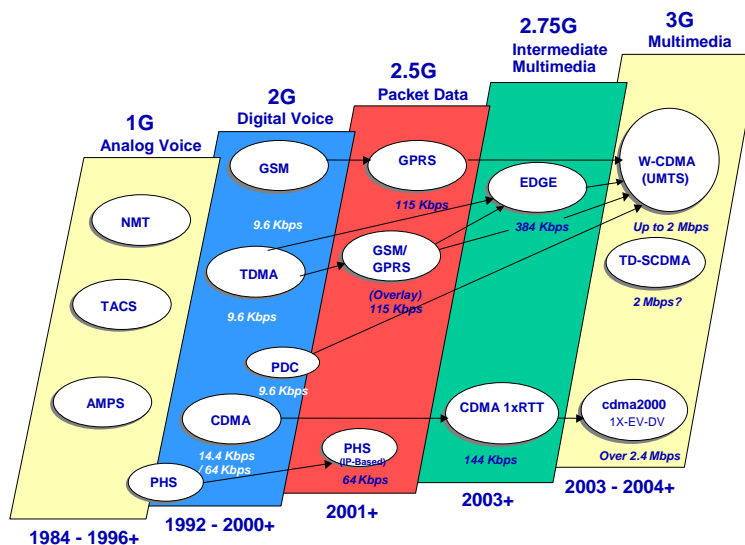


Wireless Communication Standard

1-9

2010/5/3

Ron-Yi Liu

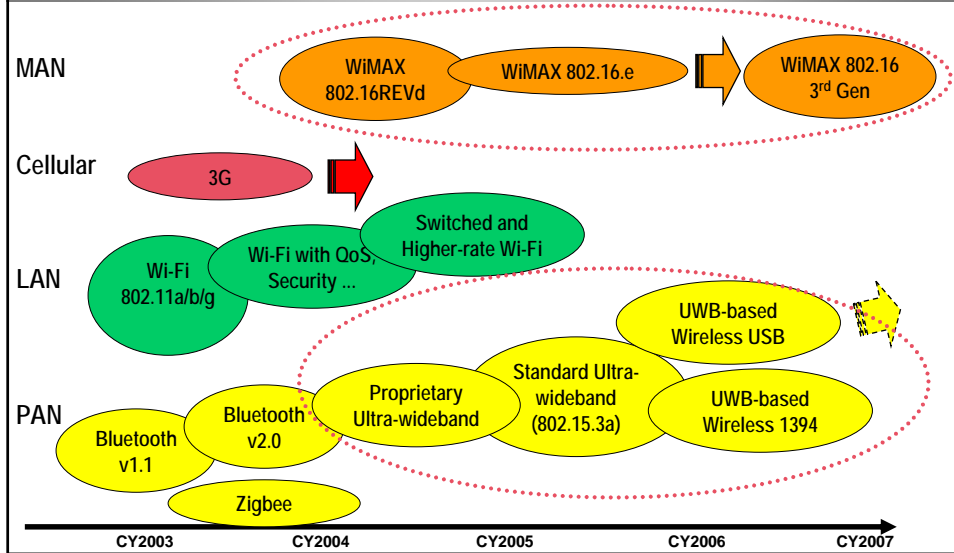


Wireless and Wire line Communication System

1-10

2010/5/3

Ron-Yi Liu

HSDPA: High-Speed Downlink Packet Access

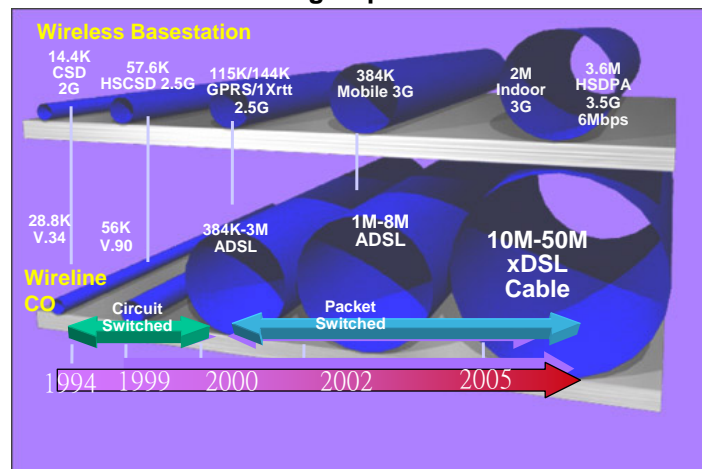


WiMAX Network Models

1-11

2010/5/3

Ron-Yi Liu

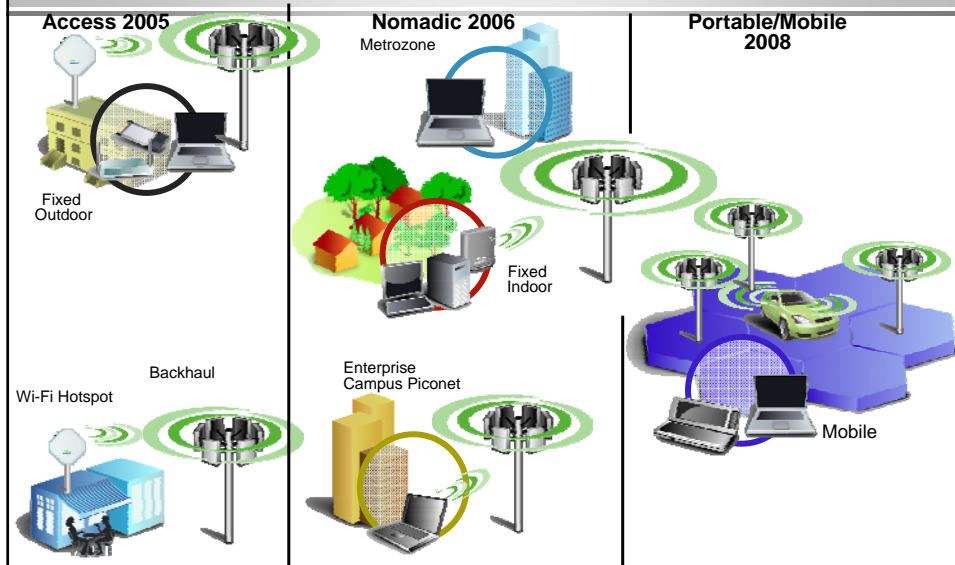


Fixed Wireless Broadband

1-12

2010/5/3

Ron-Yi Liu

 Proprietary solutions moving to WiMAX standard :



Range Km:

- Up to 3KM in Urban
- Up to 10KM in Suburban
- Up to 30KM in Rural

802.16 Communication Specification

1-13

2010/5/3

Ron-Yi Liu

標準	802.16	802.16-2004	802.16-2005
Bit Rate(Mbps)	32-134 (in 28MHz channel bandwidth)	Up to 75 (in 20MHz channel bandwidth)	Up to 15 (in 5MHz channel bandwidth)
Mobility	Fixed	Fixed, Portable	Fixed, Portable, Mobility
Spectrum(GHz)	10-66	<11	<6
Channel Conditions	Line of Sight only	Non Line of Sight	Non Line of Sight
Channel Bandwidths(MHz)	20,25,28	Scalable 1.5-20	Scalable 1.5-20
Typical Cell Radius (KM)	2-5	7-10 (Max Range 50)	2-5
Completed	2001/12	2004/06	2005/12

The Comparison of WiMAX and HSDPA

1-14

2010/5/3

Ron-Yi Liu


	802.16-2004	802.16e	HSDPA
Data Rate	75 Mbps/20MHz	15 Mbps/5MHz	14.4Mbps/5MHz
Cell Radius	5 km	5 km	2 km
Mobility	Portable	Up to 100 km/hr	Up to 120 km/hr
Freq. Allocation	2~11GHz	2~6GHz	1.9~2.2GHz
Spectral Efficiency	3.75 bps/Hz	3 bps/Hz	2.9 bps/Hz
Access Technology	OFDM	OFDM/OFDMA	CDMA
Modulation	BPSK, QPSK, 16QAM, 64QAM	BPSK, QPSK, 16QAM, 64QAM	BPSK, QPSK, 16QAM

The Comparison of Mobility

1-15

2010/5/3

Ron-Yi Liu

 


Reference Source : WiMAX Forum

Broadband Communication Network

1-16

2010/5/3

Ron-Yi Liu

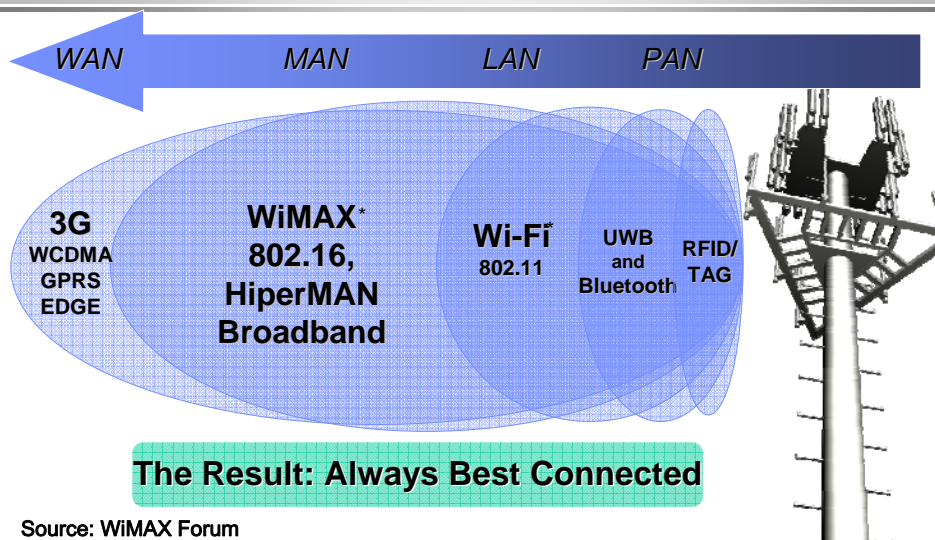

The Result: Always Best Connected

Source: WiMAX Forum

Vision: Wireless Communication

1-17

2010/5/3

Ron-Yi Liu




CMOS Wireless LAN Chip Design

1-18

2010/5/3

Ron-Yi Liu


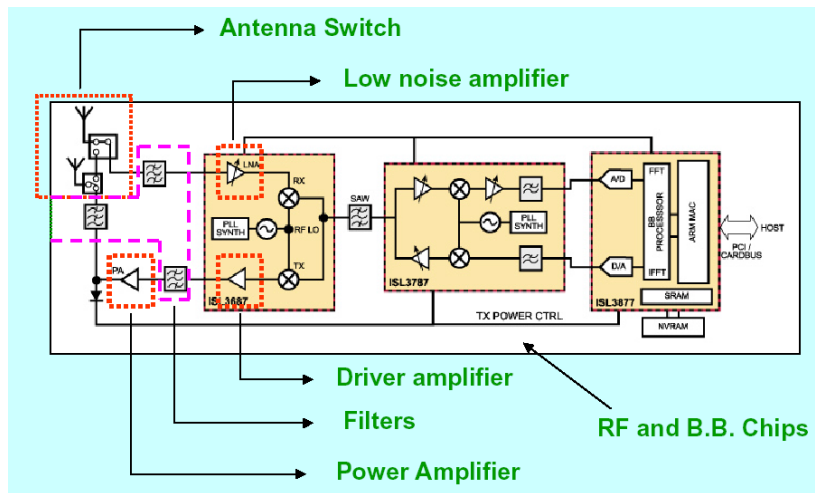


Design Abstraction Levels

1-19

2010/5/3

Ron-Yi Liu

 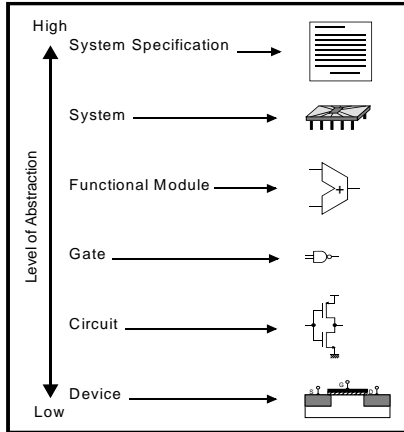


CMOS Hierarchical Modeling and Design

1-20

2010/5/3

Ron-Yi Liu

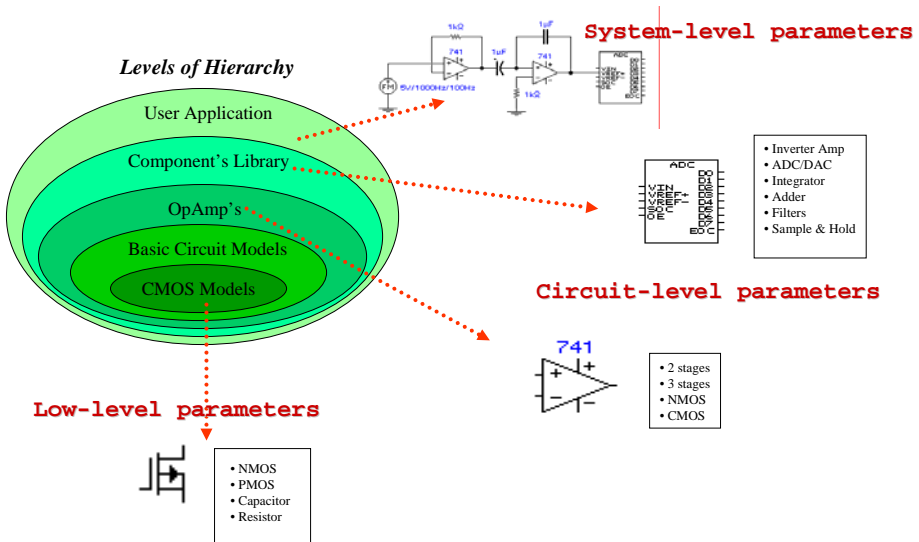

CMOS Analog Circuit Design Process

1-21

2010/5/3

Ron-Yi Liu

■ Design Specifications.



■ Topology Selection.

■ Circuit Sizing.

■ CMOS Layout.

Function: Band Pass Pass Filter
 Specifications: BW = 50 KHz
 $W_o = 679$ Hz
 Pass Atten = -3dB
 Stop Atten = -10dB
 Constraints: Area = 1000 μm^2
 Power = 3 mW
 $Z_{out} = 300$ ohms
 Gain = 4.5

  Style: Butterworth
 Order: 4th
 Implementation: Sallen-Key
 Operational Amp: 3-stage CMOS



Mixed-Signal System-On-Chip Integration

1-22

2010/5/3

Ron-Yi Liu

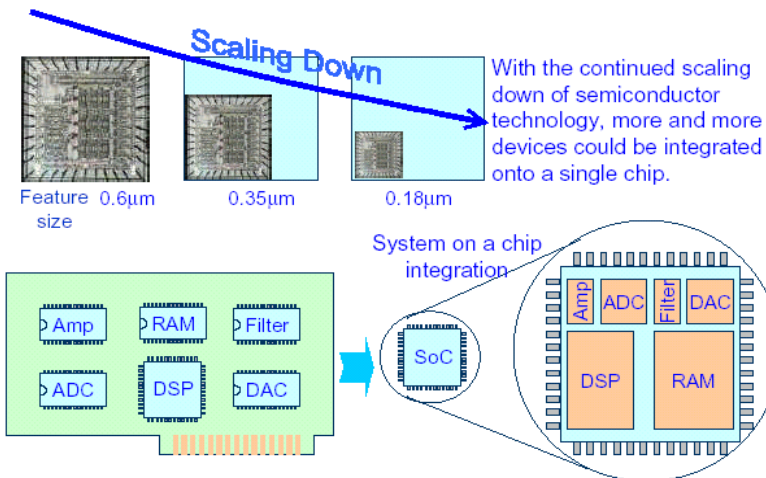


Fig. 1.2, Mixed-signal system-on-a-chip integration


10-bit CMOS ADC Chip

1-23

2010/5/3

Ron-Yi Liu

(Broadcom Corp.)

 

0.5µm, 5V

0.35µm, 3.3V

0.25µm, 2.5V


10-bit (Folding and Interpolating) ADC does not scale!

Impact of CMOS SoC Scaling

1-24

2010/5/3

Ron-Yi Liu

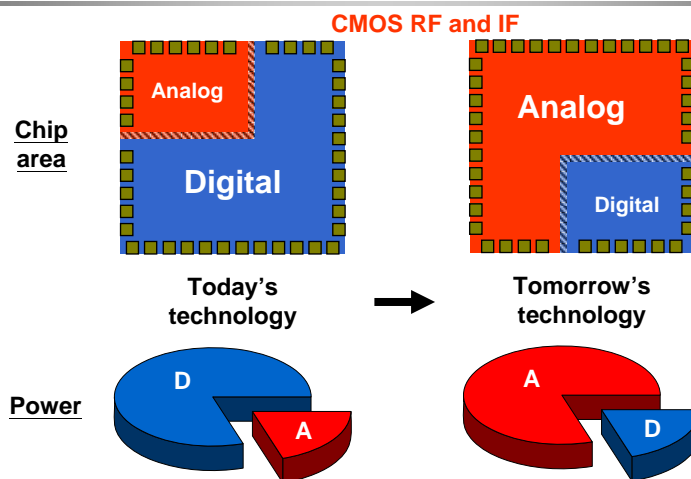


Cost dominated by Analog Circuit Design!

Communication Receiver Block Diagram

1-25

2010/5/3


Ron-Yi Liu

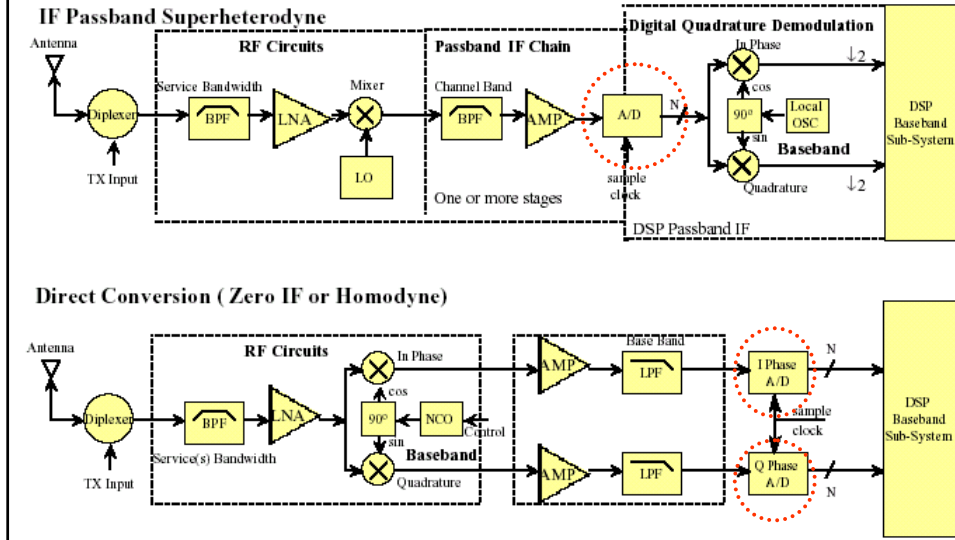

802.11 b WLAN Block Diagram

1-26

PRISM II, 11Mbps Chip Set Overview

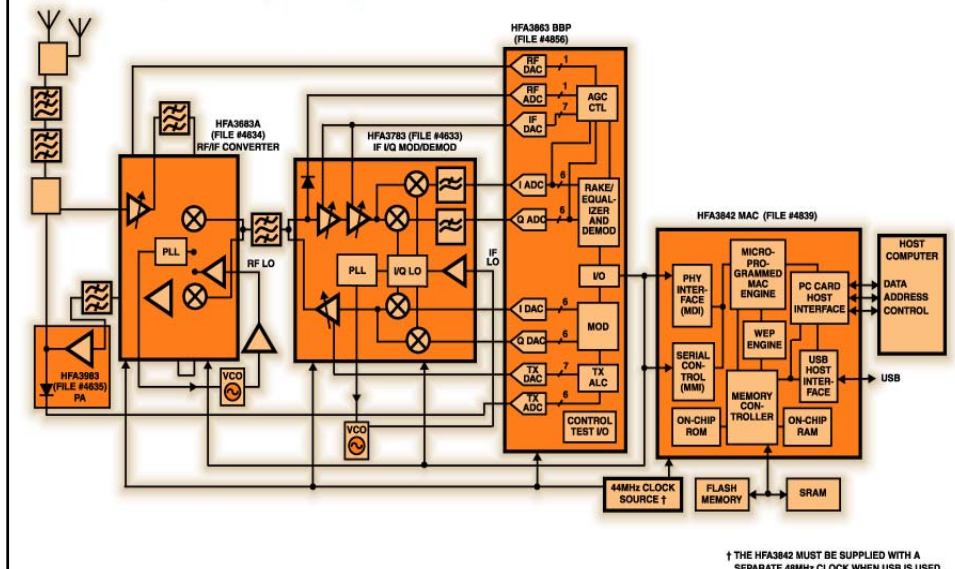


802.11a WLAN Block Diagram

1-27

2010/5/3

Ron-Yi Liu

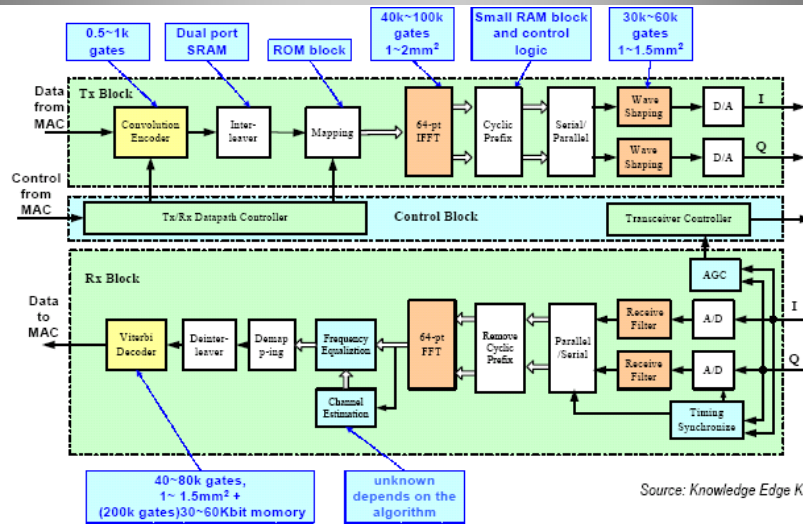


802.11a WLAN System Block Diagram

1-28

2010/5/3

Ron-Yi Liu

CPU core	Die area	Peak Power Consumption (mW/MHz)	Memory System	Clock frequency & MIPS performance
ARM9E / ARM946E-S cached processor with tightly coupled memory interfaces	4.9mm ² on 0.18μm estimated size with 16KB instruction & 4KB data caches and no TCMs Using Artisan cell library & RAM compiler	1.1 mW/MHz @ 1.8V (estimated)	Selectable I & D cache sizes: 0, 4K, 8K... 1M Selectable I & D TCM sizes: 0, 4K, 8K... 1M	150MHz on TSMC 0.18μm (worst case) 230MHz on TSMC 0.18μm (typical)

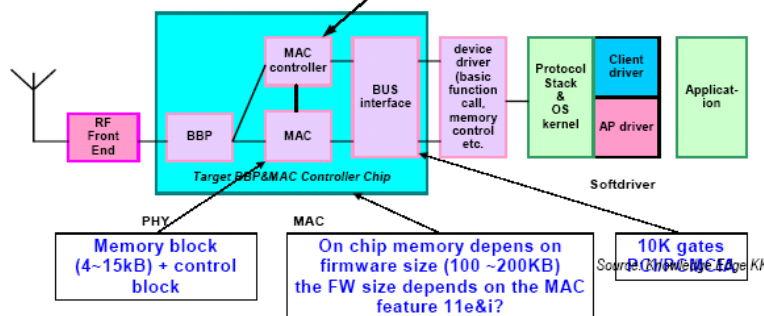

Analog Filter Design

Analog Filter

- **Analog filter** uses **analog electronic circuits** from components, such as: resistors, capacitors and Inductors, to produce the required filtering effect.


5th Order Low Pass Elliptic
 Pass Band Frequency = 10.55 MHz Stop Band Ratio = 1.613
 Pass Band Ripple = 300.0 mdB Stop Band Frequency = 17.02 MHz
 Stop Band Attenuation = 52.45 dB

- **Advantages:**

- simple circuit design.
- fast and simple realization.

- **Disadvantages:**

 - Little stable and sensitive to temperature variations.
- **Very expensive** to realize in large amounts.
- **Aged effect.**
- **Noise induced to Inductor.**



Analog Filter Design Concept

1-31

2010/5/3

Ron-Yi Liu



- ❑ This *ideal* Filter specification cannot be achieved by realizable filters because an instantaneous transition from a gain of 1 to 0 is not possible.
- ❑ Filter Synthesis: Synthesis is **generally not unique**. More than one circuit can satisfy $H(s)$.
- ❑ Today's Gm-C, Active-RC, MOS-C or switched capacitor filters are based on continuous time filters. Consequently, it is expedient to briefly review the subject of continuous time filters.
- ❑ Gm-C, Active-RC, MOS-C or Switched Capacitor Filter *approximations* which closely approximate the ideal filter but are realizable.

First Order Filter

1-32

2010/5/3

Ron-Yi Liu

Filter Type and $T(s)$	s -Plane Singularities	Bode Plot for $ T $	Passive Realization	Op Amp-RC Realization
(a) Low-Pass (LP) $T(s) = \frac{\omega_0}{s + \omega_0}$			$CR = \frac{1}{\omega_0}$ dc gain = 1	$CR_2 = \frac{1}{\omega_0}$ dc gain = $-\frac{R_2}{R_1}$
(b) High-Pass (HP) $T(s) = \frac{s\omega_0}{s + \omega_0}$			$CR = \frac{1}{\omega_0}$ High-frequency gain = 1	$CR_1 = \frac{1}{\omega_0}$ High-frequency gain = $-\frac{R_2}{R_1}$
(c) General $T(s) = \frac{\omega_0(s + \omega_1)}{s + \omega_0}$			$(C_1 + C_2)(R_1 // R_2) = \frac{1}{\omega_0}$ $C_1 R_1 = \frac{\omega_0}{\omega_1}$ dc gain = $\frac{R_2}{R_1 + R_2}$ HF gain = $\frac{C_1}{C_1 + C_2}$	$C_2 R_2 = \frac{1}{\omega_0}$ $C_1 R_1 = \frac{\omega_0}{\omega_1}$ dc gain = $-\frac{R_2}{R_1}$ HF gain = $-\frac{C_1}{C_1 + C_2}$

2nd Order LCR Resonators Circuit


1-33

2010/5/3

Ron-Yi Liu


Low-pass:
 
$$T(s) = a_2 \frac{\omega_0^2}{s^2 + s(\omega_0/Q) + \omega_0^2}$$




Bandpass:
 
$$T(s) = a_2 \frac{s(\omega_0/Q)}{s^2 + s(\omega_0/Q) + \omega_0^2}$$



Notch:
 
$$T(s) = a_2 \frac{s^2 + \omega_0^2}{s^2 + s(\omega_0/Q) + \omega_0^2}$$




Antoniou Inductance-Simulation Circuit Method

1-34

2010/5/3

Ron-Yi Liu

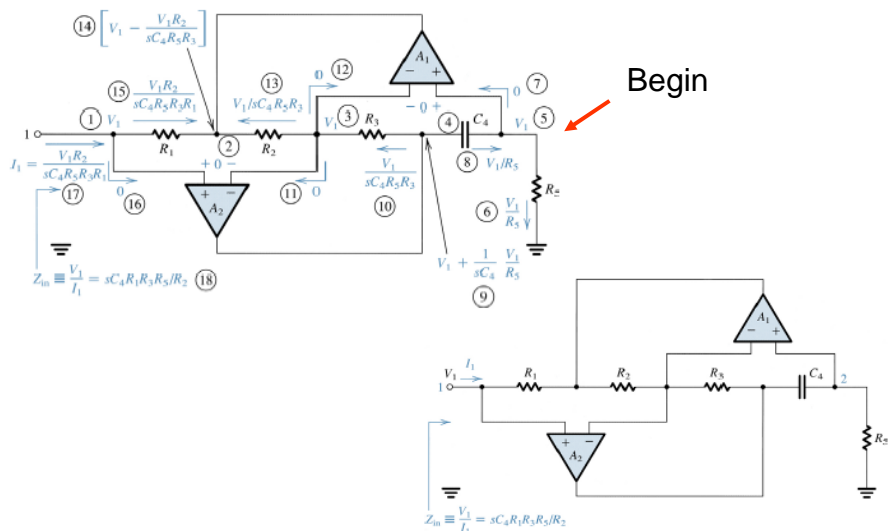


Second-Order Active Filter Design

1-35

2010/5/3

Ron-Yi Liu

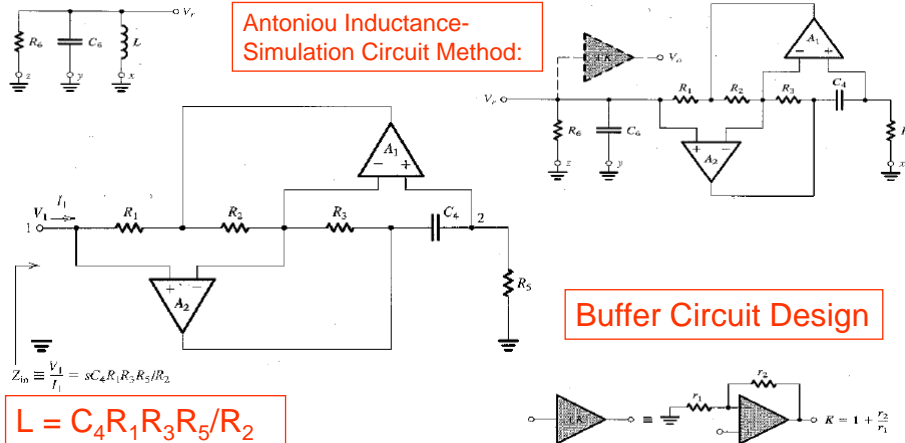■ **Replace the inductor L** : by an op amp-RC circuit that has an inductive input impedance.



Continuous-time Anti-aliasing Filter Design

1-36

2010/5/3

Ron-Yi Liu

 


Figure 5. Low-Pass Sallen-Key Circuit

$$\frac{V_O}{V_i}(lp) = \frac{K}{s^2(R_1R_2C_1C_2) + s(R_1C_1 + R_2C_1 + R_1C_2(1 - K)) + 1}$$

By letting

$$s = j2\pi f, f_c = \frac{1}{2\pi\sqrt{R_1R_2C_1C_2}}, \text{ and } Q = \frac{\sqrt{R_1R_2C_1C_2}}{R_1C_1 + R_2C_1 + R_1C_2(1 - K)}$$

參考 Project Report -5MHz CMOS Sallen-Key Low Pass Filter Circuits for DVB-H


Analog Continuous-Time Monolithic Filter

1-37

2010/5/3

Ron-Yi Liu

- **Monolithic Filter** : Low cost, good matching, reduce parasitic capacitance and automatic tuning for processing and temperature variation.
- Differential Equation from Laplace Transform: $s = j\omega$.
⇒ Higher frequency response, lower power dissipation and area
⇒ Lower Dynamic Range (DR).
- The standard **active-RC** filter: R,C and Op Amps with feedback loop.
- **MOSFET-C** filters : Op Amps and resistors often implemented with MOSFETs.
- **Gm-C** filters :resistors replaced by transconductors (used as open loop).
- **Most straightforward design!**

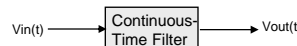

The Active-RC Filters

1-38

2010/5/3

Ron-Yi Liu

- **The drawbacks of Active-RC filters (R, C and Op Amp):**
 - ⇒ **Smaller** size than the passive filter (especially in low frequency).
 - ⇒ It is **impossible** to integrate the Resistor and Cap. into a Chip
for 1pf -> 2500 (50x50) μm^2 (4 mil²). 100pf ??
- **If : Voice band filter (0~4 KHz) :**
 - RC= 10 krad/s, C = 10pf, R=10 M Ω -> 10⁶ μm^2 (1600 mil²).
 - 1. The overall chip area is around 20,000 mil² for this circuit.
 - 2. The Poly-Si or Diffusion resistor is **nonlinear**.
 - 3. The error of resistor is 10%, and the error of capacitor is 10%
⇒ The error of RC time constant is **20% !**
 - 4. The temperature and voltage coefficients of RC time constant are *not correlated and serious*.
⇒ RC variation =~ 50% with fabrication process, temperature.
- **The Active-RC and SC Filters are relatively mature technologies.**
- **The Active-Gm/C Filter offers potential applications up to VHF.**

Active-RC Filter


1-39

2010/5/3

Ron-Yi Liu

- Moderate-to-high frequency precision (with tuning).
⇒ Small area and low power dissipation for $f < 100$ kHz.
- Feedback structure reduces sensitivity to parasitic.
- Can be realized as all biquad type circuits.

But:

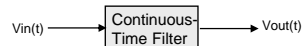

- *On-chip tuning* and corresponding circuitry is required.
- Fully-balanced-differential structures for increasing linearity.
- Op Amps and feedback circuits limit the filter -3 dB cutoff frequency. ⇐ The RC time constant in Filter must be at most *5% or 10%* of Unity Gain bandwidth to avoid the pole frequency and quality factor error.
- **Not suited for high-frequency applications !**

Filter Types

1-40

2010/5/3

Ron-Yi Liu

- Different types of polynomials :
 - ✓ Butterworth - smooth, well behaved, commonly used.
 - ✓ Chebyshev - faster roll-off but with ripple in either passband or stopband.
 - ✓ Elliptical - faster roll-off but with ripple in both passband and stopband.
 - ✓ Bessel- Approximately Linear Phase.

$$H(f) = \frac{a_0}{b_0 + b_1s + \dots + b_n s^n}$$


Characterization of Filter

1-41

2010/5/3

Ron-Yi Liu

□ A low pass filter magnitude response.

 

Three basic properties of filters.

- 1.) Passband ripple = $|T(j0) - T(j\omega_{PB})|$.
- 2.) Stopband frequency = ω_{SB} .
- 3.) Stopband gain/attenuation = $T(j\omega_{SB})$.

For a normalized filter the basic properties are:

- 1.) Passband ripple = $T(j\omega_{PB})/T(j0) = T(j\omega_{PB})$ if $T(j0) = 1$.
- 2.) Stopband frequency (called the transition frequency) = $\Omega_n = \omega_{SB}/\omega_{PB}$.
- 3.) Stopband gain = $T(j\omega_{SB})/T(j0) = T(j\omega_{SB})$ if $T(j0) = 1$.

Filter Specification by Bode Plot

1-42

2010/5/3

Ron-Yi Liu

 


Figure 9.7-2 - (a.) Low pass filter of Fig. 9.7-1 as a Bode plot. (b.) Low pass filter of Fig. 9.7-2a shown in terms of attenuation ($A(j\omega) = 1/T(j\omega)$).

Therefore,

Passband ripple = $T(j\omega_{PB})$ dB

Stopband gain = $T(j\omega_{SB})$ dB or Stopband attenuation = $A(j\omega_{PB})$

Transition frequency is still = $\Omega_n = \omega_{SB}/\omega_{PB}$



Butterworth (Maximally Flat) Filter

1-43

2010/5/3

Ron-Yi Liu

-3dB cut-off frequency

  

The roots are at

$$s_k = \epsilon^{-1/N} \exp\left(j \frac{2k+N-1}{2N} \pi\right) \quad k = 1, 2, \dots, N$$

$$|H_n(j\omega)|^2 = \frac{1}{1 + (s/j)^2} = \frac{1}{1 + (-1)^n s^{2n}}$$

$$\theta_k = 90^\circ \left(\frac{2k+n-1}{n} \right) \quad k = 1, 2, \dots, 2n$$

The transfer functions is

$$|H(j\omega)|^2 = \frac{1}{1 + \epsilon^2 \omega^{2N}}$$

N is the filter order, want **N : integer**

$$N \geq \frac{\log[(10^{0.1\alpha_{\max}} - 1)/(10^{0.1\alpha_{\min}} - 1)]}{2 \log \omega_s}$$


- **Butter worth filter:** many derivatives are zero at $\omega=0$.
- **All pole filter:** Good flatness in pass band.
- **Poor phase linearity.**
- **Moderate attenuation slope steepness.**

Butterworth Filter Approximation

1-44

2010/5/3

Ron-Yi Liu

 

EXAMPLE 9.7-1:
Determining the Order of A
Butterworth Filter
Approximation

$$|T_{LPn}(j\omega_n)| = \frac{1}{\sqrt{1 + \epsilon^2 \omega_n^{2N}}}$$

where N is the order of the approximation and ϵ is defined in the above plot.

The magnitude of the Butterworth filter approximation at ω_{SB} is given as

$$\left| T_{LPn} \left(\frac{j\omega_{SB}}{\Omega_{PB}} \right) \right| = |T_{LPn}(j\Omega_n)| = T_{SB} = \frac{1}{\sqrt{1 + \epsilon^2 \Omega_n^{2N}}}$$

This equation in terms of dB is useful for finding N given the filter specifications.

$$20 \log_{10}(T_{SB}) = T_{SB} (dB) = -10 \log_{10}(1 + \epsilon^2 \Omega_n^{2N})$$

Poles and Quadratic Factors of Normalized LP Butterworth Function

1-45

2010/5/3

Ron-Yi Liu

Table 9.7-1 - Pole locations and quadratic factors ($s_n^2 + a_1 s_n + 1$) of normalized, low pass Butterworth functions for $\epsilon = 1$. Odd orders have a product ($s_n + 1$).

N	Poles	a_1 coefficient
2	$-0.70711 \pm j0.70711$	1.41421
3	$-0.50000 \pm j0.86603$	1.00000
4	$-0.38268 \pm j0.92388$ $-0.92388 \pm j0.38268$	0.76536 1.84776
5	$-0.30902 \pm j0.95106$ $-0.80902 \pm j0.58779$	0.61804 1.61804
6	$-0.25882 \pm j0.96593$ $-0.96593 \pm j0.25882$ $-0.70711 \pm j0.70711$	0.51764 1.93186 1.41421
7	$-0.22252 \pm j0.97493$ $-0.90097 \pm j0.43388$ $-0.62349 \pm j0.78183$	0.44505 1.80194 1.24698
8	$-0.19509 \pm j0.98079$ $-0.83147 \pm j0.55557$ $-0.55557 \pm j0.83147$ $-0.98079 \pm j0.19509$	0.39018 1.66294 1.11114 1.96158
9	$-0.17365 \pm j0.98481$ $-0.76604 \pm j0.64279$ $-0.50000 \pm j0.86603$ $-0.93969 \pm j0.34202$	0.34730 1.53208 1.00000 1.87938
10	$-0.15643 \pm j0.98769$ $-0.89101 \pm j0.45399$ $-0.45399 \pm j0.89101$ $-0.98769 \pm j0.15643$ $-0.70711 \pm j0.70711$	0.31286 1.78202 0.90798 1.97538 1.41421

Chebyshev Filter

1-46

2010/5/3

Ron-Yi Liu

 


Figure 9.7-5

The magnitude of the normalized, Chebyshev, low-pass, filter approximation can be expressed as

$$|T_{LPn}(j\omega_n)| = \frac{1}{\sqrt{1 + \epsilon^2 \cos^2[N \cos^{-1}(\omega_n)]}}, \quad \omega_n \leq 1$$

and

$$|T_{LPn}(j\omega_n)| = \frac{1}{\sqrt{1 + \epsilon^2 \cosh^2[N \cosh^{-1}(\omega_n)]}}, \quad \omega_n > 1$$

where N is the order of the filter approximation and ϵ is defined as

$$|T_{LPn}(\omega_{PB})| = |T_{LPn}(1)| = T_{PB} = \frac{1}{\sqrt{1 + \epsilon^2}}$$


N is determined from $20 \log_{10}(T_{SB}) = T_{SB}(\text{dB}) = -10 \log_{10}\{1 + \epsilon^2 \cosh^2[N \cosh^{-1}(\Omega_n)]\}$

Chebyshev (Equip-Ripple) Filter

1-47

2010/5/3

Ron-Yi Liu

 

- Distribute the magnitude error in the **passband** or **stopband**.

Chebyshev

Inverse Chebyshev

$$|H(j\omega)|^2 = \frac{1}{1 + \epsilon^2 C_N^2(\omega)}$$

$$|H(j\omega)|^2 = \frac{\epsilon^2 C_N^2(1/\omega)}{1 + \epsilon^2 C_N^2(1/\omega)}$$

- Less order N than Butterworth filter (due to sharper TB).

Chebyshev Filter

1-48

2010/5/3

Ron-Yi Liu

Chebyshev Polynomial :


$$C_N(\omega) = \begin{cases} \cos[N \cos^{-1}(\omega)] & \text{for } \omega \leq 1 \\ \cosh[N \cosh^{-1}(\omega)] & \text{for } \omega > 1 \end{cases}$$

$$= 2\omega C_{N-1}(\omega) - C_{N-2}(\omega)$$

N is the filter order, want

$$N \geq \frac{\cosh^{-1}(\delta/\epsilon)}{\cosh^{-1} \omega_s} \approx \frac{\ln(2\delta/\epsilon)}{\ln(\omega_s + \sqrt{\omega_s^2 - 1})}$$

•Ellipse Pole location

 

- Good steepness of the attenuation slope. $(\frac{\sigma_k}{\sinh a})^2 + (\frac{w_k}{\cosh a})^2 = 1$

- Poor phase linearity (delay distortion), and pass band flatness.

$$Q_k = \frac{w_k}{2\sigma_k}$$

- Inverse Chebyshev filters (with transmission zeros in the stop band): have better phase and lower Q (but less sensitive to component tolerance).

Poles and Quadratic Factors of Normalized LP Chebyshev Function

1-49

2010/5/3

Ron-Yi Liu

Table 9.7-2 - Pole locations and quadratic factors ($a_0 + a_1 s_n + s_n^2$) of normalized, low pass Chebyshev functions for $\epsilon = 0.5088$ (1dB).

N	Normalized Pole Locations	a_0	a_1
2	$-0.54887 \pm j0.89513$	1.10251	1.09773
3	$-0.24709 \pm j0.96600$ -0.49417	0.99420	0.49417
4	$-0.13954 \pm j0.98338$ $-0.33687 \pm j0.40733$	0.98650	0.27907
5	$-0.08946 \pm j0.99011$ $-0.23421 \pm j0.61192$ -0.28949	0.98831	0.17892
6	$-0.06218 \pm j0.99341$ $-0.16988 \pm j0.72723$ $-0.23206 \pm j0.26618$	0.99073	0.12436
7	$-0.04571 \pm j0.99528$ $-0.12807 \pm j0.79816$ $-0.18507 \pm j0.44294$ -0.20541	0.99268	0.09142


Elliptic (Cauer) Filter

1-50

2010/5/3

Ron-Yi Liu

transmission zeros

 

Narrower TB

The transfer functions is

$$|H(j\omega)|^2 = \frac{1}{1 + \epsilon^2 R_N^2(\omega)}$$

$$\alpha_{\min} = 10 \log[1 + \epsilon^2 R_N^2(\omega_s)]$$

• **Best steepness** of the attenuation slope.

• **Complex elliptic function (by MATLAB).**

• **Poor phase linearity.**

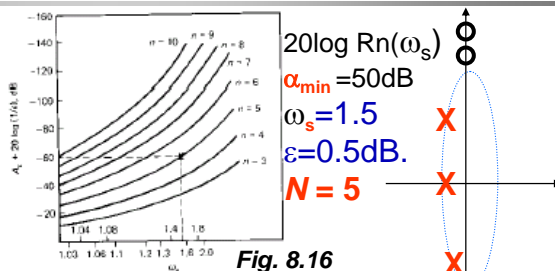


Fig. 8.16
Design curve

where

$$R_N(\omega) = k \prod_{i=1}^{N/2} \frac{\omega^2 - (\omega_s/\omega_{z_i})^2}{\omega^2 - \omega_{z_i}^2} \text{ for } N \text{ even}$$

$$= k \omega \prod_{i=1}^{(N-1)/2} \frac{\omega^2 - (\omega_s/\omega_{z_i})^2}{\omega^2 - \omega_{z_i}^2} \text{ for } N \text{ odd}$$

In the stopband, if $\epsilon^2 R_N^2(\omega) \gg 1$,

$$20 \log \frac{\delta}{\epsilon} \approx 20 \log |R_N(\omega_s)|$$

Comparison of Classical Filter

1-51

2010/5/3


Ron-Yi Liu

- $\alpha_{\max} = 0.5\text{dB}$, $\omega_p = 15.9\text{ KHz}$, $\alpha_{\min} = 50\text{ dB}$, $\omega_s/\omega_p = 1.5 \Rightarrow$ Butterworth $n=17$, Chebyshev $n=8$, Elliptic filter $n=5$ (due to the narrower TB).
- **Order** : $\alpha_{\max} = 0.25\text{dB}$, $\omega_p = 100\text{ Krad/s}$, $\alpha_{\min} = 18\text{ dB}$, $\omega_s = 140\text{ Krad/s}$
 \Rightarrow Butterworth $n=11$, Chebyshev $n=5$, Elliptic filter $n=4$.

□ **Q-value :**

$\alpha_{\max} = 0.25\text{dB}$, $\alpha_{\min} = 18\text{ dB}$, $n=5$, $Q_C > Q_{IC}$.

$$Q^2_C = 1.573Q^2_{IC} - 0.1434$$

 


- **Circuit realization** : Generally, the order of Analog active filter N is limited below 10. The order is better in the range of 4 ~ 6.

Comparison of Classical Low Pass Filter

1-52

2010/5/3

Ron-Yi Liu

 


- Butterworth is the most popular response. It has no ripple in the pass or stop.
- Chebyshev response has more roll off than Butterworth.
- Inverse Chebyshev response has ripple in the stop band, and therefore has a lot of rejection near the corner frequency, but the rejection bounces back, and there is some passage in the stop band.
- Elliptical response combines the characteristics of Chebyshev and inverse Chebyshev, having ripple in the pass band and in the stop band. Like the inverse Chebyshev, the stop band rejection has some bounce back.
- Bessel response has less rolloff in the stop band than the other types, and is not as flat in the pass band.

Transfer functions of different filter types (all 4th order)

1-53

2010/5/3

Ron-Yi Liu

 

LP Filter Response : 2MHz

1-54


2010/5/3

Ron-Yi Liu

Magnitude:

Phase

Group Delay

 


LP Filter : Poles and Zero

1-55

2010/5/3

Ron-Yi Liu

 

Biquad and Ladder Filter Design

1-56

2010/5/3

Ron-Yi Liu

- **Biquad filters : Sensitivity and Noise in key issue.**
 - ✓ Higher sensitivity of component variations.
 - ✓ Easier to compute - divide problem into subproblems (cascade-second order filters such as: Butterworth, Chebyshev, Elliptic (Cauer) and Bessel (linear Phase) etc.).
 - ✓ Active elements : R, C and Op Amp.
 - ✓ 5th order Biquad : 1st + Hi-Q + Low-Q
 - ✓ 6th order Biquad : Hi-Q + Mid-Q + Low-Q
 - ✓ SCF, Gm-C Filter.
- **Ladder filters : Good choice!!**
 - ✓ Low sensitivity to component variations.
 - ✓ Not Easy to compute - by Table filters such as: Butterworth, Chebyshev, Elliptic (Cauer) and Bessel (linear Phase) etc.
 - ✓ Passive elements such as : R, L and C.
 - ✓ SCF, Gm-C Filter.

Digital Filter

1-57

2010/5/3

Ron-Yi Liu

- **Digital Filters** : DSP

⇒ Discrete time system by Difference Equation.

⇒ A/D introduces quantization noise.

⇒ Z-transform, Z^{-1} is the unity delay.

⇒ With Programmability and larger Dynamic Range (DR).



1-58

2010/5/3

Ron-Yi Liu

Switched Capacitor Filter Design

The Concept of SC Networks

1-59

2010/5/3

Ron-Yi Liu

- **The most popular approach in analog signal processing since early 1970.**
- **Compatibility with standard CMOS process technologies.**
- **No A/D and D/A converters** ⇒ **Analog Sampled Data (Discrete time signal) system with DSP concept.**
- **Accurate discrete-time frequency (0.1%)** ⇒ **since the Filter coefficients (time constant) determined by Capacitor Ratio and clock (sampling) frequency.**
- **Very Good voltage linearity.**
- **Good Process and Temperature characteristics.**
- **Switched Capacitor Network's (SCN) main Applications :**
 - ✓ Filter, ADC and DAC, Sigma-Delta Modulators, Gain-stages in DAC, Voltage-Control Oscillators, Decimation and Interpolation Filter.

Switched Capacitor Circuits


1-60

2010/5/3

Ron-Yi Liu

Sampled-data Signal:

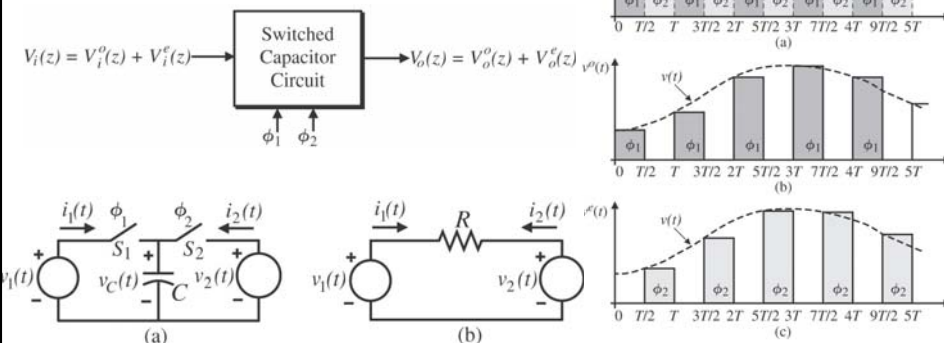Continuous amplitude, discrete time signal.




Resistor Emulation!

Basic Switched Circuits Concept

1-61

2010/5/3

Ron-Yi Liu

 

□ SC simulated **Positive** resistor :

$$\phi_1: V_{c1} = V_1 \quad \phi_2: V_{c1} = V_2$$

$$\Rightarrow \Delta Q = C(V_1 - V_2)$$




$f_s \equiv \frac{1}{T}$ Equivalent average current in each clock :

$$\Delta Q/T = i_{avg} = C(V_1 - V_2)/T = C f(V_1 - V_2) = (V_1 - V_2)/R$$

$$\Rightarrow \boxed{R_{eq} = T/C = 1/(Cf_s)} \quad f_s: \text{clock frequency.}$$

□ Example 9.1-1 : Allen's Book

   $f_s = 100 \text{ KHz}, C = 10 \text{ pf} \Rightarrow R = 1 \text{ M}\Omega$, less area .



CMOS Switches


1-62

2010/5/3

Ron-Yi Liu

- **NMOS** or **PMOS** switch only $\Rightarrow v_1$ or $v_2 (= v_{DD} - v_{in} = 0 \sim 4 \text{ v})$ due to the body effect or $(= v_{DD} - v_{tp} = 1 \sim 5 \text{ v})$. \Rightarrow **CMOS** switch.
- **CMOS** switch can cancel the nonlinear effects from **Nonlinear parasitic cap**, **channel charge injection**, **clock feed through**, **Noise** and **capacitive coupling** from logic signal to each side of the CMOS switch.

Section 12.2: Razavi's book.

 


On-resistance in CMOS Switch circuits

1-63

2010/5/3

Ron-Yi Liu

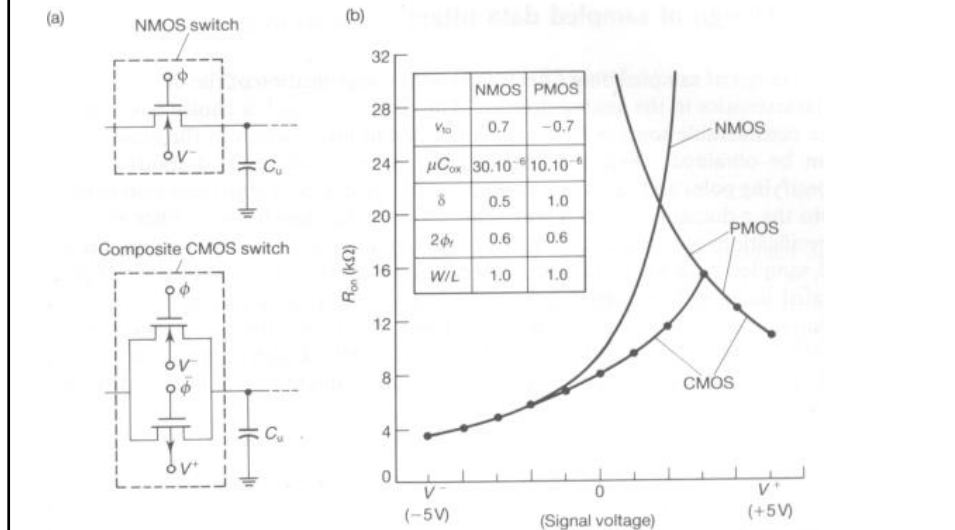


Switched Capacitor Filter

1-64

2010/5/3

Ron-Yi Liu

 - **Switched Capacitor (Sampled-Data) Filters** : Discrete (sampled) time but continuous (analog) in amplitude.
 - ✓ Resistors replaced by switched capacitors.
 - ✓ Parasitic Capacitance insensitive.
 - ✓ Very high precision without tuning.
 - ✓ Fully-balanced-differential structures for high dynamic range (DR).
 - ✓ Small area and low power dissipation.
- **Much more widely used!**




Basic Concepts of SCF

1-65

2010/5/3

Ron-Yi Liu

- **General Switched Capacitor Networks (SCNs) :**
- **Ideal capacitors, ideal voltage-controlled voltage sources (VCVS), ideal switches and sampled-data voltage inputs.**
- **VCVS \Rightarrow Freq. indep. gain amps or infinite gain Op Amp.**
 - \Rightarrow Typically, the sampled-data voltage inputs is only single, not multiple.
 - \Rightarrow The input may be a continuous or Sampled-and-Hold (S/H) signal.
 - \Rightarrow The voltages of nonideal switches, non-ideal OP AMPs, non-ideal cap. should be considered as *second order* effects.

 

Sallen-Key Low-Pass Filter

Switched Capacitor Filter

1-66

2010/5/3

Ron-Yi Liu


- **Switched Capacitor (Sampled-Data) Filters :** Discrete (sampled), But:
 - ✓ Needs clock circuits.
 - ✓ Sample-data effects : Needs Anti-aliasing Filter required to prevent the high frequency signal input.
 - ✓ Reconstruction (smoothing) filter is required to smoothen the staircase signal and high frequency noise.
 - ✓ **S-to-Z-transform** by Bilinear and LDI (Realize functions with no CT equivalent)
 - ✓ Inefficient use of Op Amp's bandwidth: $f_{\text{cutoff}}/F_s \gg 1$ for $\text{Sinc}(x) = \sin(x)/x$ (Sampled/Hold) Effect.
 - ✓ Not suited for high-frequency applications (less than 50MHz LP Filter).

The s-z Transformation

1-67

2010/5/3

Ron-Yi Liu

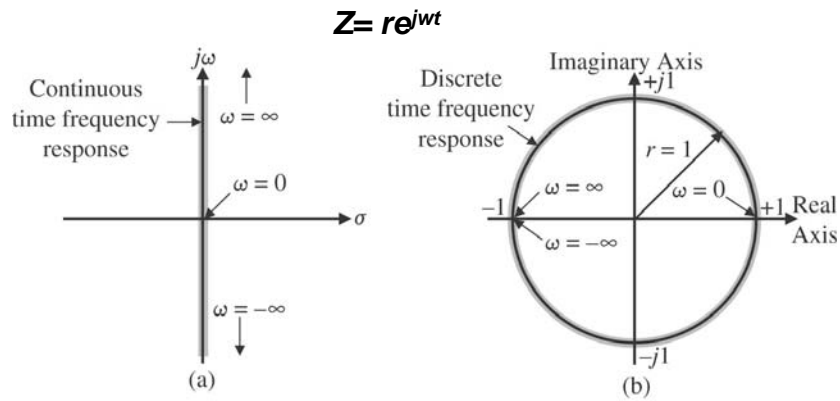


The LDI s-z Transform Method

1-68

2010/5/3

Ron-Yi Liu

 - The LDI-z transformation (midpoint integration):
 - ⇒ **Warping effect (frequency axis expand)!**
 - ⇒ **Approximately design the LC ladder filter.**




The Bilinear s-z Transform Method

1-69

2010/5/3

Ron-Yi Liu

 - The Bilinear-z transformation :
 - ⇒ **Warping effect (frequency axis shrink)!**
 - ⇒ **Exactly design the LC ladder filter.**
- Preserve both the loss and phase response in pass band. ⇒ **Good for linear phase (Bessel) filter design!**



The s-z LDI and Bilinear Transform

1-70

2010/5/3

Ron-Yi Liu

- If Input signal frequency $f \ll F_s$ sampling frequency
 - ⇒ **No need of $\sin x/x$ compensation and prewarping.**

- However, The LDI or Bilinear Transformation have the **phase error due to the frequency-axis warping.**


 


Fig. 1.15 Warping effect introduced by bilinear and LDI transformations (adapted from

Frequency-Axis Warping of Bilinear Transform ¹⁻⁷¹

2010/5/3

Ron-Yi Liu

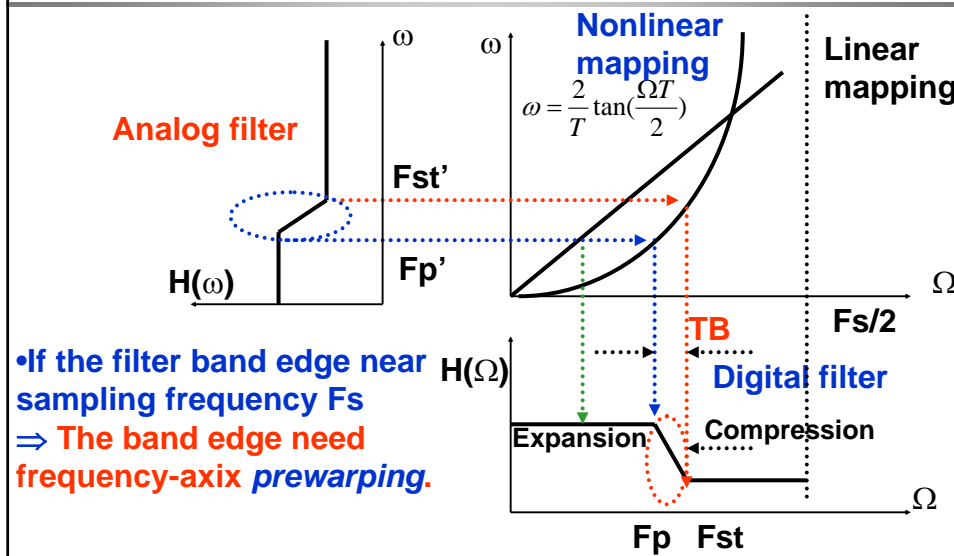


Higher-order Filter Design : Cascade Approach ¹⁻⁷²

2010/5/3

Ron-Yi Liu

Higher-order Filter Design

 

□ **Cascade Approach: Simpler** Z-domain digital Filter synthesizer (Design according to the filter spec. and sampling frequency).

Issues:

1. Higher Filter coefficient sensitivity structure.
2. The Coefficient arrangement in each block.
3. Noise problems.

Z-domain digital Filter :

FDS Synthesizer by SPW

1-73

2010/5/3

Ron-Yi Liu


- **Simpler** Z-domain digital Filter synthesizer (according to the filter spec. and sampling frequency). ←However, this architecture will have **higher Filter coefficient sensitivity**.
- The biquadratic circuit's $H(z)$ for 6th order **(2-2-2)** or 5th order **(1-2-2)** can be designed in the Z-domain directly (choose the Chebyshev, Elliptic, Bessel filter type) in **SPW or Matlab**.
- Realized (Synthesized) the Z-domain coefficients by the capacitor's ratio of SC biquadratic circuits such as Laker's SC blocks from $H(z)$.
- Simulated again by **SWITCAP II** for spec. checking (include the **dynamical capacitor scaling** in each op amp output, and **minimum capacitor scaling** in each virtual GND).
- Overall SC mixed-signal circuits layout (Be careful in choosing **unit capacitor, C_u**).

SCF Design Flow

1-74

2010/5/3

Ron-Yi Liu

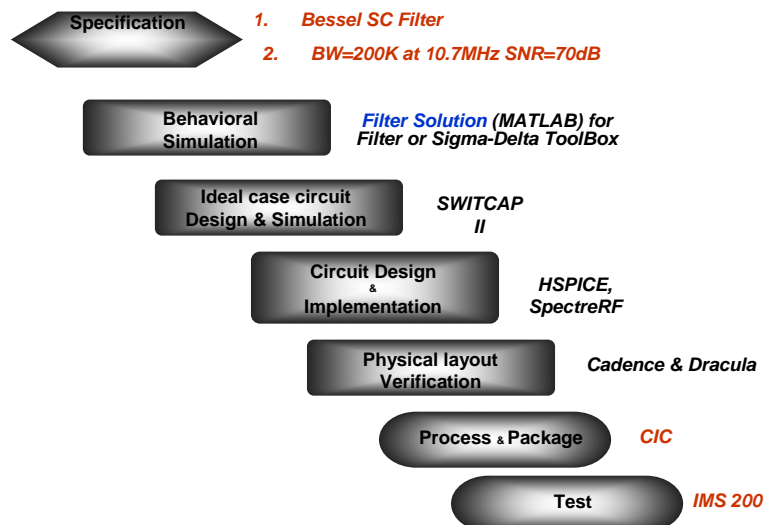



Simulation of SC circuits

1-75

2010/5/3

Ron-Yi Liu

- SCN is a **LTV (Linear Time Varying)** system and not easily simulated by **HSPICE** for **frequency response**.
- SCN is a **Linear System** with less HD.
- SC integrator **approximates** the ideal **continuous-time integrator** when the input frequency is much less than the sampling frequency.
- **HSPICE case** : **This tool is not a good simulation method!** (Example 9.7-5 Allen's book, page 541, 569~580) so you better use **SWITCAP II** and **SpectreRF**.


 
 


5th-order Chebyshev LP Filter Design

1-76

2010/5/3

Ron-Yi Liu

  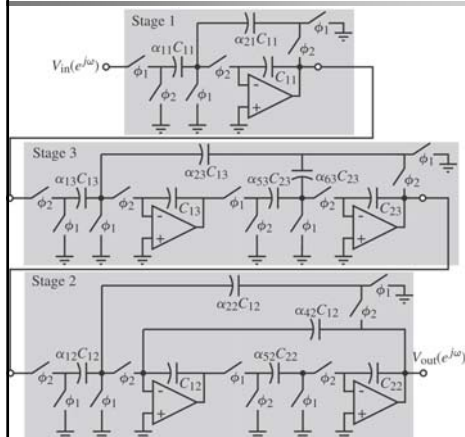

- There appears to be a **sinx/x effect** on the **magnitude** which causes the **passband specification** to not be satisfied.
- **Stopband specifications met**

5th-order Chebyshev LP Filter Design

1-77

2010/5/3

Ron-Yi Liu

Switcap2 Input File (The exact same results were obtained as for SPICE)

```

TITLE: EXAMPLE 9-7-5
OPTIONS:
NOLIST;
GRID;
END;
TIMING:
PERIOD 50E-6;
CLOCK CLK 1 (0 25/50);
END;
SUBCKT (1 100) STG1;
S1 (1 2) #CLK;
S2 (2 0) #CLK;
S3 (3 4) #CLK;
S4 (3 0) #CLK;
S5 (5 100) #CLK;
S6 (5 0) #CLK;
CL11 (2 3) 0.0909;
CL21 (3 5) 0.0909;
EI (100 0 0 4) 1E6;
END;
SUBCKT (200 300) STG2;
S1 (200 2) #CLK;
S2 (2 0) #CLK;
S3 (3 0) #CLK;
S4 (3 4) #CLK;
S5 (6 5) #CLK;
S6 (6 0) #CLK;
S7 (7 0) #CLK;
S8 (7 8) #CLK;
S9 (200 9) #CLK;
S10 (9 0) #CLK;
CL13 (2 3) 0.2058;
CL23 (3 9) 0.2058;
CL63 (9 7) 0.1471;
CL13 (4 5) 1;
END;
SUBCKT (100 200) STG3;
S1 (100 2) #CLK;
S2 (2 0) #CLK;
S3 (3 0) #CLK;
S4 (3 4) #CLK;
S5 (6 5) #CLK;
S6 (6 0) #CLK;
S7 (7 0) #CLK;
S8 (7 8) #CLK;
S9 (200 9) #CLK;
S10 (9 0) #CLK;
CL13 (2 3) 0.2058;
CL23 (3 9) 0.2058;
CL63 (9 7) 0.1471;
CL13 (4 5) 1;
END;
CL53 (6 7) 0.2058;
C23 (8 200) 1;
EI (5 0 0 4) 1E6;
E2 (200 0 0 8) 1E6;
END;
CIRCUIT;
X1 (1 100) STG1;
X2 (100 200) STG3;
X3 (200 300) STG2;
V1 (2 0);
END;
ANALYZE SSS;
INFREQ 1 3000 LIN 150;
SET V1 AC 1.0 0.0;
PRINT vdb(100) vp(100);
PRINT vdb(200) vp(200);
PRINT vdb(300) vp(300);
PLOT vdb(300);
END;

```

Micropower Low Pass Ladder Filter Simulation - Circuit and Input Description

1-78


2010/5/3

Ron-Yi Liu

```

TITLE: Switch-Capacitor Low-pass Filter
TIMING:
PERIOD 1E-5;
CLOCK CLK 1 (0 1/2);
END;
CIRCUIT;
S1 (1 2) #CLK;
S2 (2 0) #CLK;
S3 (3 0) #CLK;
S4 (4 0) #CLK;
S5 (5 0) #CLK;
S6 (6 0) #CLK;
S7 (3 7) #CLK;
S8 (4 19) #CLK;
S9 (5 9) #CLK;
S10 (6 10) #CLK;
S11 (8 14) #CLK;
S12 (14 0) #CLK;
S13 (11 15) #CLK;
S14 (15 0) #CLK;
S15 (12 16) #CLK;
S16 (16 0) #CLK;
S17 (13 17) #CLK;
S18 (17 0) #CLK;
S19 (18 10) #CLK;
S20 (18 0) #CLK;
C1 (2 3) 2.625;
C2 (3 4) 2.375;
C3 (4 5) 2.125;
C4 (5 6) 1.25;
C5 (3 14) 2.125;

```

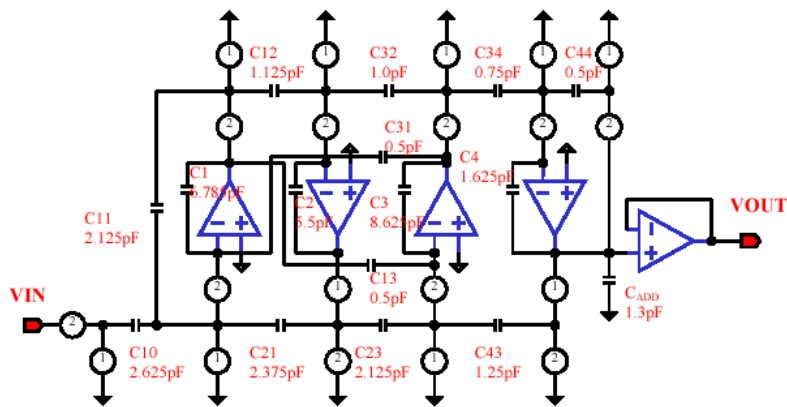

Low Pass Ladder Filter Simulation Result

1-79


2010/5/3

Ron-Yi Liu

```

C6 (7 8) 6.875;
C7 (19 11) 5.5;
C8 (9 12) 8.625;
C9 (10 13) 1.625;
C10 (10 0) 1.3;
C11 (14 15) 1.125;
C12 (15 16) 1.0;
C13 (16 17) 0.75;
C14 (17 18) 0.5;
C15 (7 12) 0.5;
C16 (8 9) 0.5;
E1 (8 0 0 7) 7413;
E2 (19 0 0 11) 7413;
E3 (12 0 0 9) 7413;
E4 (10 0 0 13) 7413;
V1 (1 0);
END;

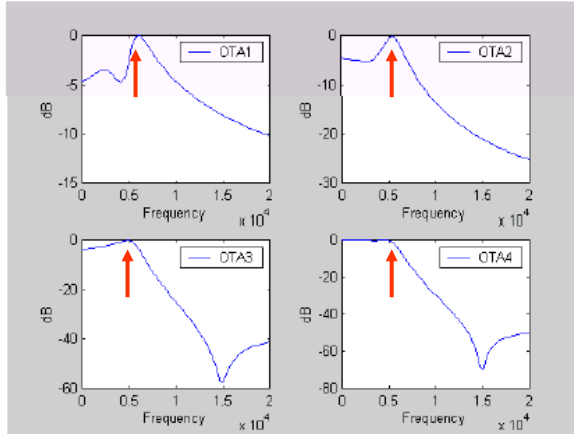ANALYZE SSS;
INFREQ 0.001 20000 LIN 50;
SET VI AC 1 0;
PRINT VDB(8) VDB(19) VDB(12) VDB(10);
PLOT VDB(8) VDB(19) VDB(12) VDB(10);
END;
    
```



- Dynamic scaling.
- Minimum Capacitor Spread Scaling.

The Dynamic Range (DR) Scaling of Capacitors

1-80


2010/5/3

Ron-Yi Liu

The Optimization of the dynamic range using Scaling Procedures :

⇒ Improve the actual performance and avoid the saturation of each *OP AMP*.

- Let all branches connected to the *output* terminal O_{Ai} be modified such that their Q/V_i (transfer functions) in F_4 , F_5 and F_6 are multiplied by a positive factor K .
- **This can be achieved by multiplying all capacitors in these branches by K_i .**
- Since the input branches and their voltages were unchanged, the charge flowing in the feedback branch is remain at its original value.
- **The voltage scaling does not affect charge flowing from the scaled branch to the rest of the circuits.** ⇒ Only $V_i \rightarrow V_i/K_i$, all other voltages or charges are not affected.
- $V_{max}/A_p > V_{in,max}$, A_p : *passband gain*, $V_{in,max}$ is the max. input signal which the SCF can handle without excessive nonlinear distortion.

 

$$V_i^*(Z) = \Delta Q_4(Z) / [K_i F_4(Z)] = V_i(Z) / K_i$$

$$\Delta Q_5^* = F_5^*(Z) V_i^*(Z) = K_i F_5(Z) V_i(Z) / K_i$$

$$= F_5(Z) V_i(Z) = \Delta Q_5$$

□ all Op-Amp outputs should be scaled to 0dB.

The Optimum Dynamic Scaling of Capacitors in SCFs

1-81

2010/5/3

Ron-Yi Liu

- For maximum dynamic range, all Op-Amp outputs should be scaled to **0dB** such that (at its own maximum frequency) each saturates for the same input voltage level.

1. OA_2 will saturate before OA_5 , because $|V_2| > |V_3|$ for $w \sim w_2$.

2. $V_{in,max} = V_{max}/A_2$, $A_2 = |V_{p2}/V_{in}|$, $A_p = |V_{p5}/V_{in}| \Rightarrow A_2 = A_p |V_{p2}/V_{p5}|$

3. $V_{in,max} = V_{max}/A_2 = [V_{max}/A_p] |V_{p5}/V_{p2}| < V_{max}/A_p$. since $|V_{p5}/V_{p2}| < 1$.


\Rightarrow Maximum Vin decrease, then Dynamic range decrease.

- Reduce V_2 by scaling, $V'_2(w) = V_2(w)/K_2$, $K_2 = V_{p2}/V_{p5}$.

$\Rightarrow V'_2$ has a peak value V'_{p2} (which is equal to V_{p5}), then $V_{in,max} = V_{max}/A_p$.

- Similarly, $K_3 = V_{p3}/V_{p5} < 1$, $K_1 = V_{p1}/V_{p5} < 1$, $K_4 = V_{p4}/V_{p5} < 1$.

 - Scaling for optimum dynamic range may also reduce the sensitivity to the finite Op-Amp gain effects



The Minimum Capacitor Scaling of SCFs

1-82

2010/5/3

Ron-Yi Liu

- The Optimization of the Min. Capacitor Scaling Procedures :

\Rightarrow Reduce the overall silicon area (The total capacitor value in SCFs).

- Let all branches connected to the input terminal OA_i be multiplied by a positive factor m_i .

$\Rightarrow C_i \rightarrow m_i C_i$, Q_n ($n=1, 2, 3$ and 4) $\rightarrow \Delta Q'_n = m_i \Delta Q_n$

$$V_i^* = \frac{\Delta Q'_4}{F_4} = \frac{m_i \Delta Q_4}{m_i F_4} = \frac{\Delta Q_4}{F_4} = V_i$$

\Rightarrow The input charges Q_5 and Q_6 also remain the same.


- The scaling by m_i make all output voltages unchanged. (Only the charges in the scaled branches multiplied by m_i .)

\Rightarrow Effective in reducing the capacitor spread and the total capacitance in SCFs.

- $C_{i,min}$ among all capacitors contained in these four branches located.

\Rightarrow All capacitors contained in these four branches are multiplied by $m_i = C_{min}/C_{i,min}$.

 - The smallest capacitance become C_{min} and all Op-Amp voltages remain unaffected.



After voltage scaling, all capacitors are scaled to minimum values in order to save area

If $\frac{C_{min}}{\min\{C_{i,1}, \dots, C_{i,n}, C_r\}} = m_j$, then $C_{i,1}, C_{i,2}, \dots, C_{i,n}, C_r$ are given the new values $m_j C_{i,1}, m_j C_{i,2}, \dots, m_j C_{i,n}, m_j C_r$

Capacitor Layout in SC circuits

1-83

2010/5/3

Reference: Martin's book, pp.108~112. *Ron-Yi Liu*

□ Since the thickness of S_iO_2 is 700~5,000 Å, typical MOS capacitor $C = 0.25\sim 0.5$ fF/ μm^2 . Typical **capacitor spread** is $C_{min}/C_{max} = 20\sim 40$ for SC circuits.

- Square type unit capacitor C_u in SCF \Rightarrow for the same area-perimeter ratio.
- common-centroid layout. \Rightarrow Low sensitivity to the oxide thickness gradient.

□ Non-unit-sized capacitor : $1 \sim 2 C_u$.

□ The overall capacitors connected to Op Amp's output is the loading capacitor CL of Op Amp spec. \Rightarrow remember to define the CL in Op carefully before Op Amp design.

DR scaling Min Cap
DR scaling

Table 1: Capacitor values

Switched capacitors			Integrating capacitors				
C_{10}	1	2	C_{11}	2.3764	2.0877	4.18	
C_{11}	1	0.8785	1.75	C_{12}	0.7773	1.6957	13.3
C_{12}	1	2.1815	4.37	C_{13}	0.4850	1.5964	1.59
C_{13}	1	0.8785	6.89	C_{14}	3.9820	3.9820	7.22
C_{14}	1	3.2916	5.96	C_{15}	5.1474	2.8387	9.05
C_{15}	1	-1	1	C_{16}	0.3519	0.9680	10.53
C_{16}	1	-1	2	C_{17}	0.8313	0.7422	1.73
C_{17}	1	0.8785	1.59	C_{18}	2.2910	0.9791	1.96
C_{18}	1	0.5515	1	Transmission zeros			
C_{19}	1	1	3.19	C_A	0.5684	0.3135	1
C_{10}	1	0.5515	6	C_B	0.5684	-0.4993	1
C_{11}	1	2.7510	8.77				
C_{12}	1	0.5515	1				
C_{13}	1	0.4274	1.36	Cmax/Cmin=81			
C_{14}	1	0.8929	1.79	Cmax/Cmin=13			
C_{15}	1	0.4274	1				
C_{16}	1.1650	0.4979	1				
C_{17}	0.2311	-0.1275	1				
C_{18}	0.1046	0.0919	1				

SWITCAP II Simulator

1-84

2010/5/3

Ron-Yi Liu


- **Faster and very accurate** Simulated by SWITCAP II for Filter specification checking include:
 - The **frequency-domain** and time-domain analysis in addition to Sampler and Hold effects.
 - The **finite Gain and Bandwidth** effects in Op Amp, and **finite Ron resistance** in SWITCH.
 - The **dynamical capacitor scaling** in each op amp output, and **minimum capacitor scaling** in each virtual GND.
 - Noise and Capacitor sensitivity Analysis.
 - SC Filter simulation is according to the **capacitor's ratio** and **sampling frequency** F_s in frequency domain and time domain. \leftarrow unit capacitor is relative (not absolute) numerical, such as : $C_u=1.0$ (5 μm X 5 μm ~10 μm X 10 μm).

Double-Pole-Double-Throw Switch

1-85

1998/6/19

Ron-Yi Liu

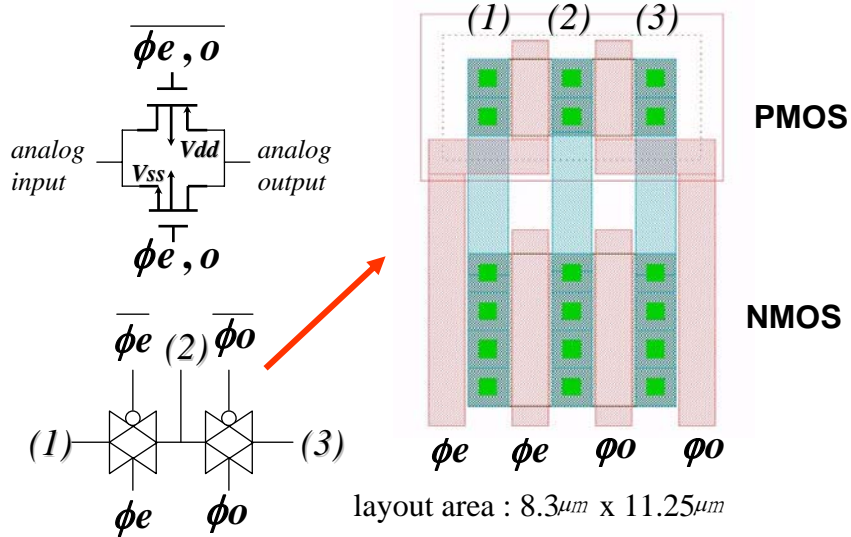


VCO Circuit Structure

1-86

2010/5/3

Ron-Yi Liu

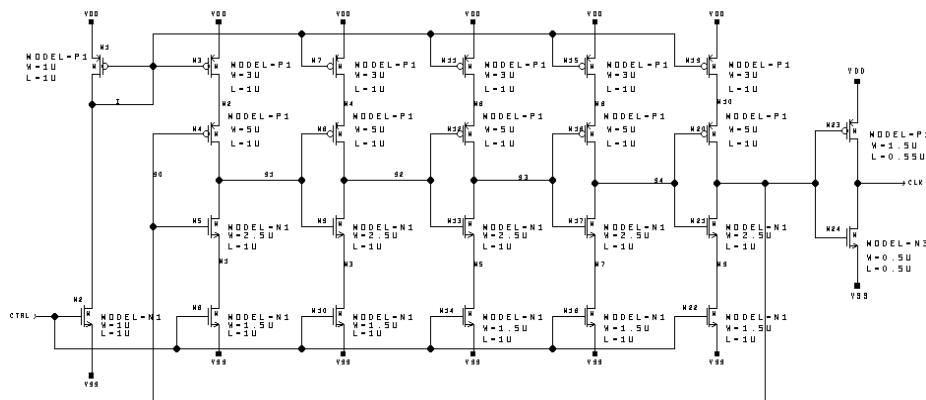


VCO Circuits Layout and HSPICE Simulation Results

1-87

2010/5/3

Ron-Yi Liu

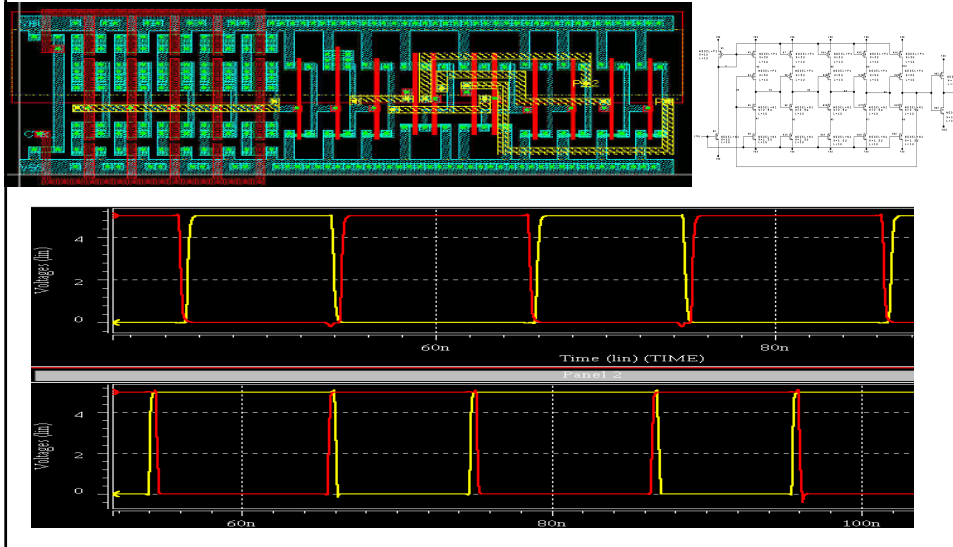

The Four-Phase Non-overlap Clock Generator


1-88

1998/6/19

Ron-Yi Liu

- Duty cycle=40~45%, to avoid **clock overlapping**.
- Delay circuits is by even number of inverters.
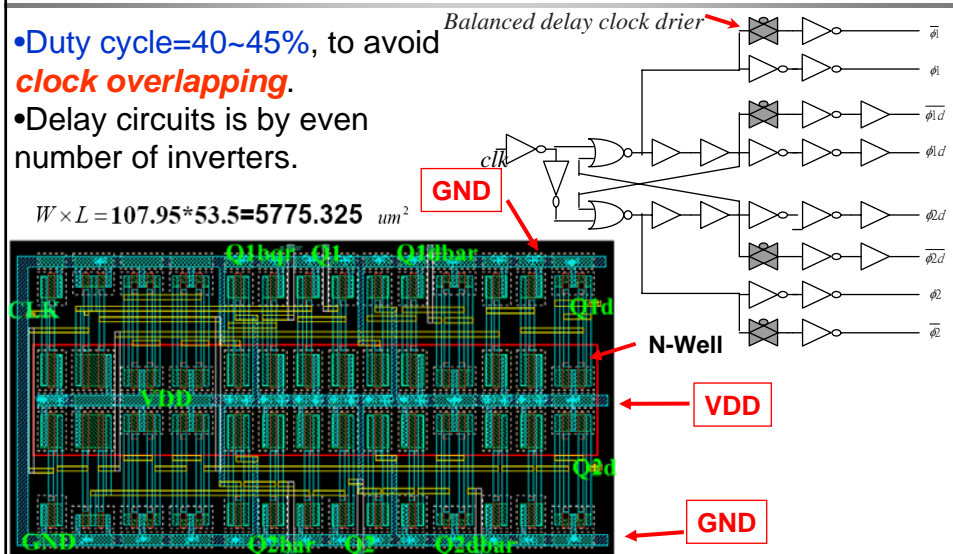
$$W \times L = 107.95 \times 53.5 = 5775.325 \text{ } \mu\text{m}^2$$



The Simulation Results of Four-phase Non-overlap Clock Generator



1-89

1998/6/19

Ron-Yi Liu

Post-simulation

CMOS 0.5um 2P2M process

  

layout area : 138 μm x 48 μm

- duty cycle = 41.2 %
- delay = 2.5 ns
- power = 1.595nW

Design and Layout of SC Circuits

1-90

2010/5/3

Ron-Yi Liu


- Check LP, BP and HP Filter band edge, Sampling frequency about: signal magnitude's S/H effect and frequency-axis prewarping.
- Design by Cascade approach (directly in Z-domain) or Ladder approach (analog s-domain)?
- Check the Filter spec. (order, pass- and stop-band ripple, phase, transition band, ..) about filter type of Butterworth, Chebyshev, Elliptic,..from CAD (MATLAB, Filter solution,..) for H(z) [biquadratic structure] or H(s) [RLC-ladder structure].
- Realize the SC (Fully Differential) circuits from digital H(z) or analog H(s).
- Simulate the SC circuits by SWITCAP II and check the dynamic scaling for these capacitors around each Op amp's output and minimum capacitor scaling for these capacitors around each Op amp's input.
- Check the Capacitor's spread and unit capacitor.
- Check Op Amp design to meet the required Gain and Bandwidth.
- Overall SC circuits Layout and post-simulation.

SC Circuit Layout (Single Ended-Op Amp)

1-91

2010/5/3

Ron-Yi Liu

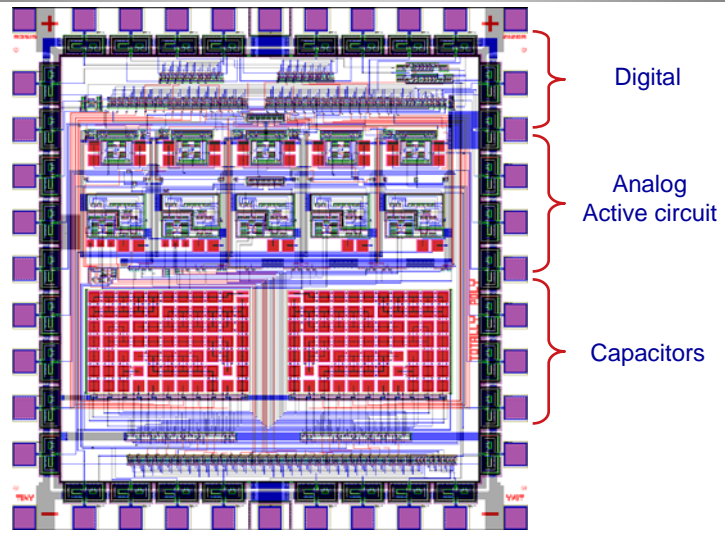


The Differential-Type SC Integrators

1-92

2010/5/3

Ron-Yi Liu

 - This a standard and important strategy, especially in low-voltage processes.
- A new degree of freedom :
 => The single-ended circuits: A positive gain with output delayed $Z^{1/2}$ (numerator).
 => The differential circuits: The sign of **gain** may be chosen arbitrarily by interchanging **input** or **output** terminals



$$V_{out}^+ = -V_{out}^- = A_v(V_{in}^+ - V_{in}^-)$$

$$H_1(z) = (V_{out}^+ - V_{out}^-) / (V_{in}^+ - V_{in}^-)$$

$$= -\frac{C_1}{C_2} \frac{Z^{1/2}}{(Z^{1/2} - Z^{-1/2})} \quad \text{Phase-2 output}$$

$$H_2(z) = -\frac{C_1}{C_2} \frac{Z^{-1/2}}{(Z^{1/2} - Z^{-1/2})} \quad \text{Phase-1 output}$$

Distortion Cancellation in Differential-SC Integrators

1-93

2010/5/3

Ron-Yi Liu

 


Fig. 10.17 Demonstrating that even-order distortion terms cancel in fully differential circuits if the distortion is symmetrical around the common-mode voltage. Here, the common-mode voltage is assumed to be zero.

- The signals are the **difference** between two voltages in symmetrical circuits of common-mode type.
- Noise as a common-mode signal and does not affect the signal.
- Only very small odd-order distortion terms. \Rightarrow Better **CMRR** and **PSRR**.
- Better noise rejection (Against offset and charge injection).
- Better **frequency response** and Slew Rate (SR).


The Basic Fully-Differential Switched-Capacitor Integrator

1-94

1998/6/19


Ron-Yi Liu

• Noninverting integrator

 

$$H(z) \equiv \frac{V_o(z)}{V_i(z)} = \left(\frac{C_g}{C_i}\right) \frac{z^{-1}}{1-z^{-1}}$$

• Inverting integrator

 

$$H(z) \equiv \frac{V_o(z)}{V_i(z)} = -\left(\frac{C_g}{C_i}\right) \frac{1}{1-z^{-1}}$$

- **Symmetrically Balanced and More components** (switches, capacitors and OP Amps).
- **Thermal noise** increases due to the added components and switching operations.
- Need **common-mode feedback** or **common-mode bias circuits**.


LDI Fully-Differential

1-95

Switched-Capacitor Integrator

Ron-Yi Liu

2010/5/3

 

•It is a very simple integrator.


Inverting Integrator

$$H(z) \equiv \frac{Vo(z)}{Vi(z)} = -\left(\frac{Cg}{Ci}\right) \frac{1}{1-z^{-1}}$$

Non-Inverting Integrator

$$H(z) \equiv \frac{Vo(z)}{Vi(z)} = \left(\frac{Cg}{Ci}\right) \frac{z^{-1}}{1-z^{-1}}$$

 •It is very important in the design of (fully differential) Sigma-Delta ADC design .




Biquadratic fully differential SCF Filter

1-96



Ron-Yi Liu

2010/5/3

 

■ 1-V differential input at two circuit frequencies.

■ Clock frequency is 40 kHz.

  

Filter output for 1-V differential input: (a) 500 Hz and (b) 2 kHz.


The Floor Placement of Four-order Sigma-Delta SC Modulator

1-97

2010/5/3

Ron-Yi Liu

(Fully differential-Op Amp)

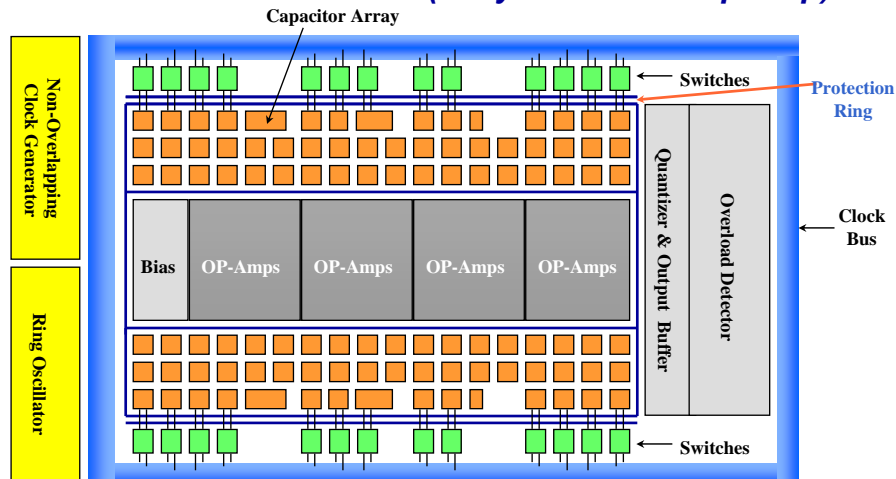

Switched Capacitor Circuits Design

1-98

2010/5/3

Ron-Yi Liu

Reference :

1. *Design of Analog CMOS Integrated Circuits*- Behzad Razavi, 2001.- Chap. 12, pp. 405-447.
2. *Switched-Capacitor Filters-Theory, Analysis and Design*- P.V.Ananda Mohan, V. Ramachandran, M. N. S. Swamy, 1995.
3. *Analog Integrated Circuit Design*- David A. Johns and Ken Martin, 1997, Chap. 10, pp. 394-444.
4. *Design of Analog integrated Circuits and Systems*- K. R. Laker and W. M. C. Sansen, 1994. Chap. 8, pp. 758-889.
5. *MOS Switched-Capacitor and Continuous-Time Integrated Circuits and Systems*- R. Unbehauen and A. Cichocki, 1991., Chap. 3, 4 and 5, pp. 172-444. 6.
6. *Analog MOS Integrated Circuits for Signal Processing*- R. Gregorian, Gabor C. Temes 1985. Chap. 5, "Switched-Capacitor Filters", pp. 265-410.
7. *Design of Analog-Digital VLSI Circuits for Telecommunications and Signal Processing*- 2nd Ed. J. E. Franca and Yannis Tsividis, 1994., Chap. 7, pp. 213-249. Chap. 8, pp. 251-288.
8. *IEEE Press, Analog MOS Integrated Circuits II*, part 1.2, pp. 159-274, 1988.
9. *IEEE Proceeding "Switched-Capacitor Filters"*, pp. 926-1005. 1983.